

## Circuit diagrams

This is the AVR Atmega Microcontroller system with external circuit blocks attached (which are their own separate circuit diagrams) that are drawn in the subsequent figures.

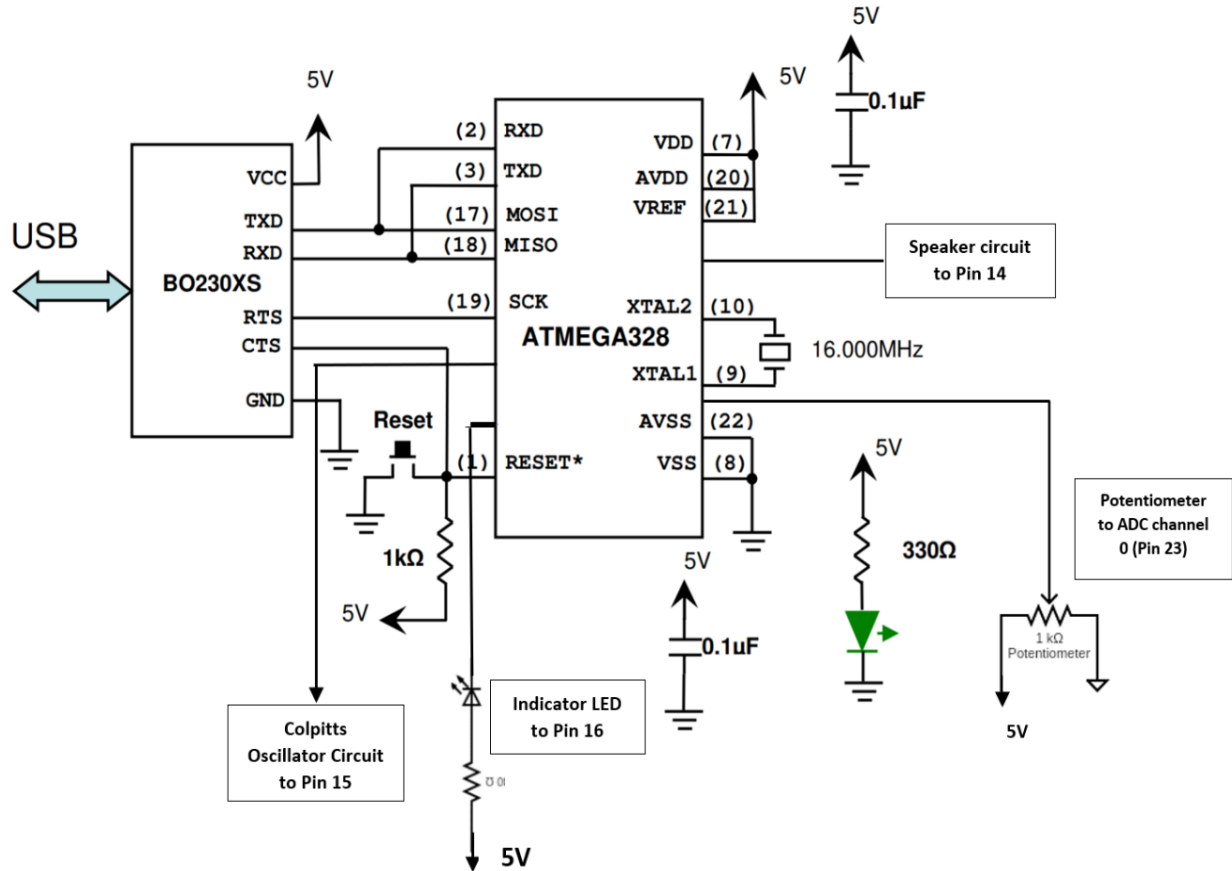


Figure 1: Metal detector circuit

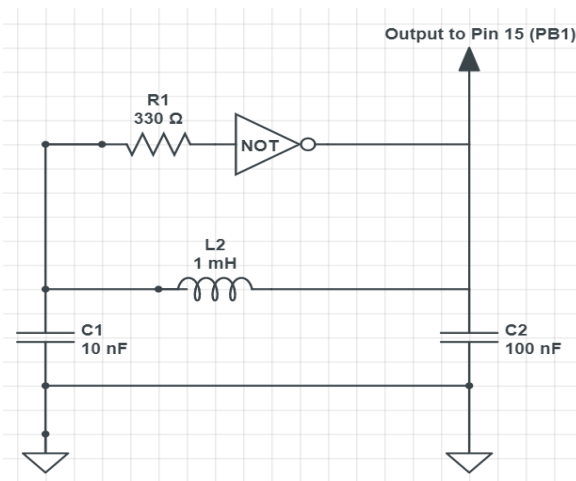


Figure 2: Colpitts Oscillator Circuit

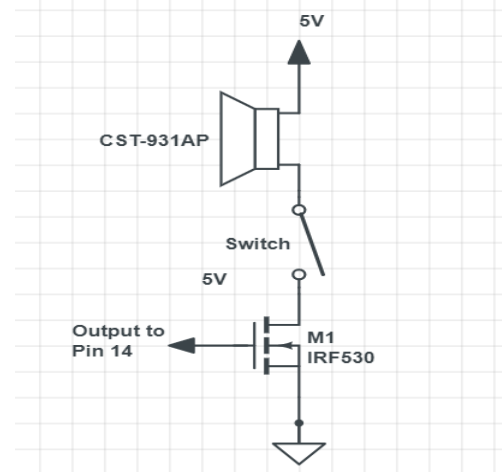


Figure 4: Speaker circuit

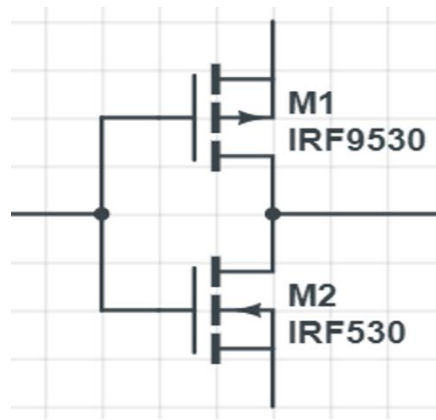


Figure 3: CMOS Inverter  
using PMOS and NMOS